



University of Moratuwa

**Department of Electronic & Telecommunication
Engineering**

EN3030 – Circuit and System Design

RISCV 32I Processor Design

Abeywickrama K.C.S.	190018V
Udayantha B.D.S	190639B
Vikasitha K.S.S.	190648C
Wijesuriya D.R.R.T	190712T

Content

- 1.** Introduction
- 2.** Design Approach
- 3.** Data Path and Control signals
- 4.** Type of Instructions
- 5.** All Possible Operations
- 6.** Control Unit
- 7.** ALU Control Unit
- 8.** ALU
- 9.** Program Counter
- 10.** Register File
- 11.** Cache memory
- 12.** Resource Usage
- 13.** Achieved performance.
- 14.** Demonstration

Introduction

The purpose of this project is to design and implement a single cycle RISC-V 32 bit CPU that supports the RV32I RISC-V ISA specification. The CPU design is required to include the instruction classes R-type, I-type, S-type, and SB-type, and to integrate with a direct mapping cache that includes a victim cache feature. Functionality, resource usage, and performance, with a special focus on reducing the overall delay are considered. The success of the project is verified by running suitable assembly programs on the designed CPU. This report provides an overview of the design and implementation process, as well as a archived performance.

Design Approach

- **Identify the instructions:** Identify all the instructions supported by the RISC-V ISA and categorize them into groups based on their functionality. This helps in understanding the operations that the processor needs to perform.
- **Decode the instruction:** Once the instruction is fetched, it needs to be decoded to determine the type of operation to be performed and the operands involved.
- **Determine the control signals:** Based on the type of operation, the control logic needs to generate the control signals to control the operations of the processor. For example, if the instruction is a load, the control logic would generate signals to read data from the memory and load it into a register.
- **Implement the control logic:** The control logic can be implemented in a programmable logic device such as a field-programmable gate array (FPGA). Verilog is used as the hardware description language. Behavioral model is used.
- **Test and debug:** Finally, the control logic is tested and debugged using test benches and run in simulators to ensure that it is functioning correctly. This involves testing the control logic with a variety of instructions and ensuring that it generates the correct control signals and check the output.
- **Physical Implementation:** Upload the synthesized design to the given Altera DE2-115 FPGA board. To display the output 7 segment display is used. Inbuilt 50 MHz clock is used as the clock source.


Single Cycle Design

To be able to run the each and every instruction in a single cycle, following approach is used
Every read operation (register/memory) implemented as combination logic (not involving the clock)

Every write operation (register/memory) implemented as sequential logic (fired on the clock)

So able to do the read and write operation in a single cycle

Data Path and Control Signals

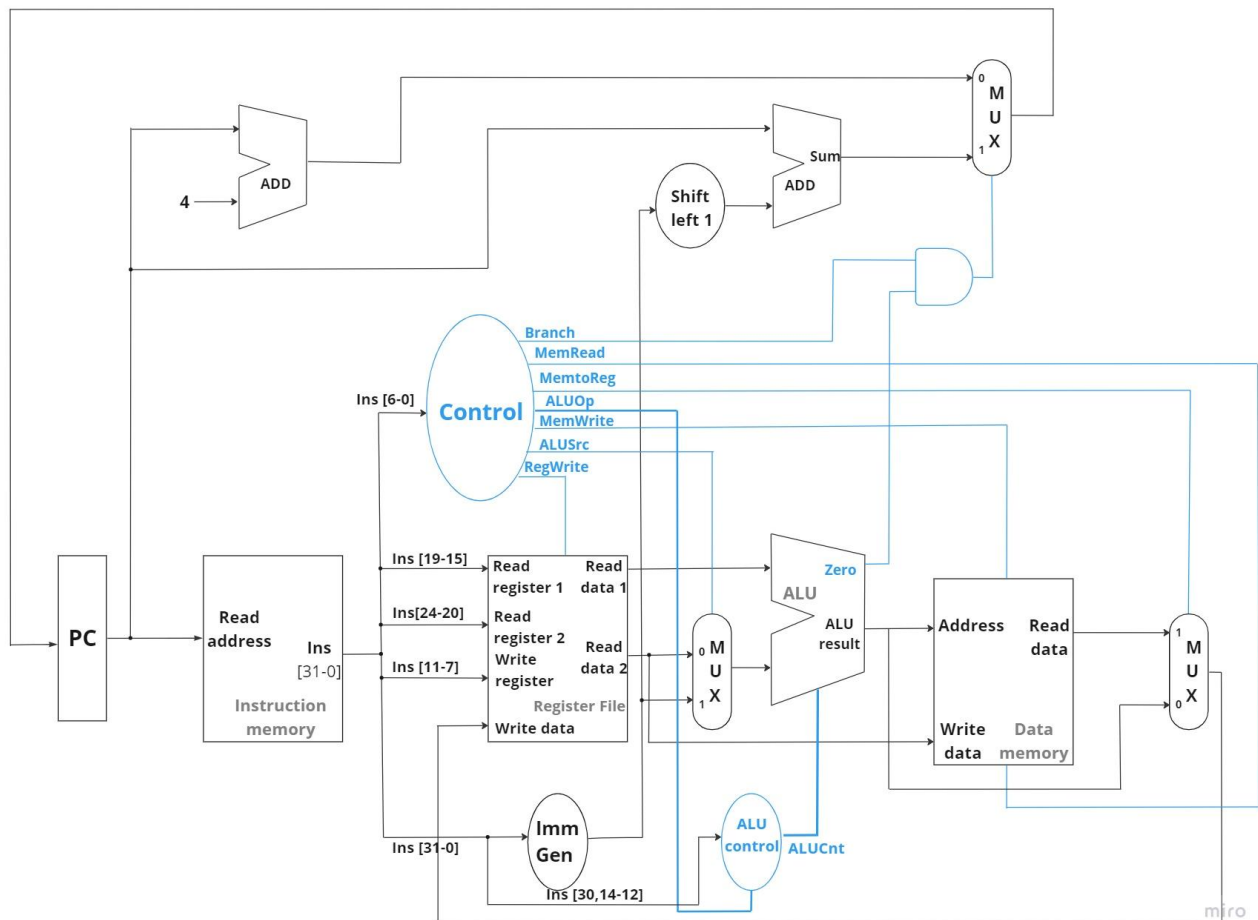

Instruction memory outputs the instruction based on the PC value. Operands, Opcode and immediates are extracted from the instruction by slicing and connecting to the relevant path. Control unit generate control instruction for each unit based on the opcode. ALU control unit generate the control signals to perform operators based on the ALUOp from Control Unit, func3 and func7 fields of the instruction. Register File, Muxes, Data Memory activated accordingly based on the control signals form Control unit. PC increment by 4 or desired immediate based on control signals

Types of Instructions

R - Type

Function 7	rs2	rs1	Function 3	rd	opcode
------------	-----	-----	------------	----	--------

I - Type

Imm[11:0]	Rs1	Function 3	rd	Opcode
-----------	-----	------------	----	--------

S - Type

Imm[11:5]	rs2	Rs1	Function 3	Imm[4:0]	opcode
-----------	-----	-----	------------	----------	--------

SB - Type


Imm[12,10:5]	rs2	rs1	Function 3	Imm[4:1,11]	opcode
--------------	-----	-----	------------	-------------	--------

ALL possible operations

All the following instructions can be run in this processor.

R – Type	I – Type	I - Type	S - type	SB - Type
add rd, rs1, rs2	addi rd, rs1, imm	lb rd, offset(rs1)	sb rs2, offset(rs1)	beq rs1, rs2, imm
sub rd, rs1, rs2	xori rd, rs1, imm	lh rd, offset(rs1)	sh rs2, offset(rs1)	bne rs1, rs2, imm
xor rd, rs1, rs2	ori rd, rs1, imm	lw rd, offset(rs1)	sw rs2, offset(rs1)	blt rs1, rs2, imm
or rd, rs1, rs2	andi rd, rs1, imm	lbu rd, offset(rs1)		bge rs1, rs2, imm
and rd, rs1, rs2	slli rd, rs1, imm	lhu rd, offset(rs1)		bltu rs1, rs2, imm
sll rd, rs1, rs2	srli rd, rs1, imm			bgeu rs1, rs2, imm
srl rd, rs1, rs2	srai rd, rs1, imm			
sra rd, rs1, rs2	slti rd, rs1, imm			
slt rd, rs1, rs2	sltiu rd, rs1, imm			
sltu rd, rs1, rs2				

Control Unit

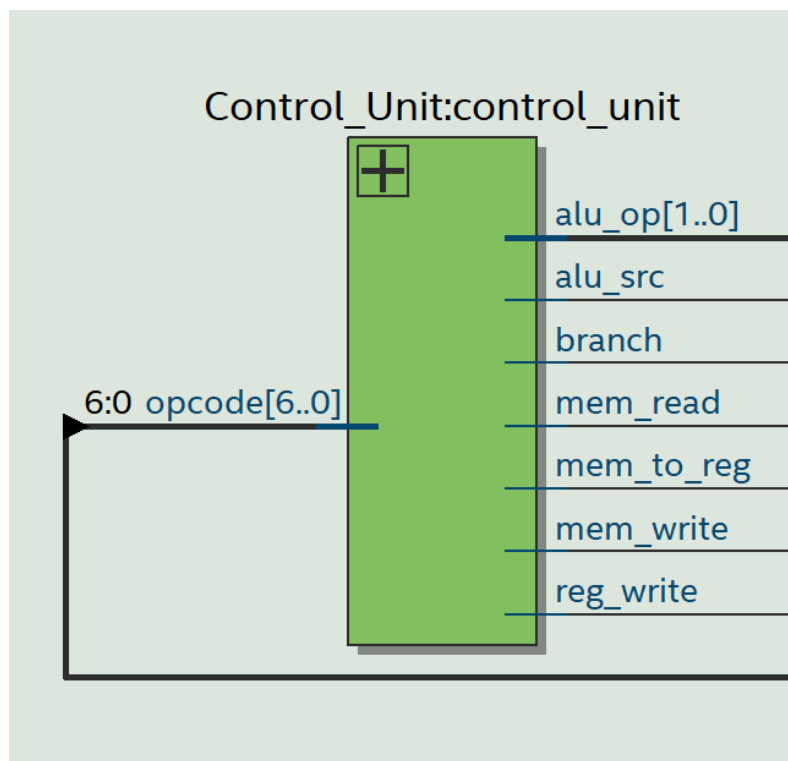

There is only one input to the control unit of this processor. It is a seven bit long binary number, and it is the opcode of the given instruction. As there are five types of instructions for this processor, it is required to have five different opcodes. Here are the five opcodes.

1. b0110011 – R type
2. b0000011 – I type (load instructions)
3. b0010011 – I type
4. b0100011 – S type
5. b1100011 – SB type

After receiving this input, the control unit identifies the instruction type and it activates some output registers. You can see the output registers of the control unit and their bit sizes below.

OUTPUTS of the control unit: -

- | | | |
|------|---|------------------------------|
| i. | ALU_OP – 2 bits controlling input to the ALU control unit | |
| ii. | alu_src | } 1 bit Control unit outputs |
| iii. | mem_to_reg | |
| iv. | reg_write | |
| v. | mem_read | |
| vi. | mem_write | |
| vii. | branch | |

ex: `case(opcode)`

7'b0110011: // R-Type

begin


alu_src = 1'b0;
 mem_to_reg = 1'b0;
 reg_write = 1'b1;
 mem_read = 1'b0;
 mem_write = 1'b0;
 branch = 1'b0;
 alu_op = 2'b10;

end

	Opcode	alu_src	mem_to_reg	reg_write	mem_read	mem_write	branch	alu_op
R	0110011	0	0	1	0	0	0	10
I	0000011	1	1	1	1	0	0	00
I	0010011	1	0	1	0	0	0	11
S	0100011	1	x	0	0	1	0	00
SB	1100011	0	x	0	0	0	1	01

Table: -Control signal values for a specific opcode

ALU control unit

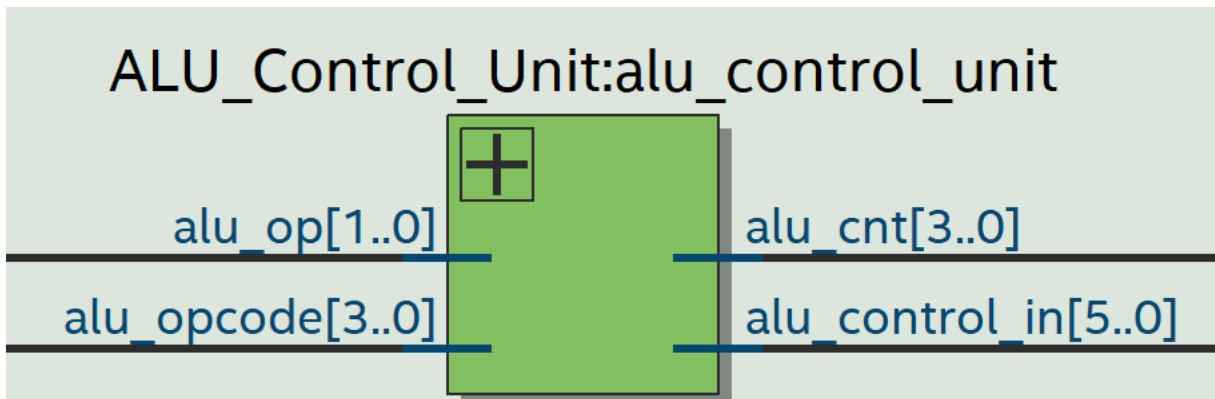

There are two inputs to the ALU control unit. They are **alu_op** and **ins[30,14:12]**. With the combination of alu_op and ins[30,14:12] we can give a command to ALU to do a defined operation.

Ex: See the appendix for the full code

//I type ALU controls for immediate operations


```
6'b11x000: alu_cnt=4'b0000; //addi
6'b11x100: alu_cnt=4'b0010; //xori
6'b11x110: alu_cnt=4'b0011; //ori
6'b11x111: alu_cnt=4'b0100; //andi
6'b110001: alu_cnt=4'b0101; //slli
6'b110101: alu_cnt=4'b0110; //srli
6'b111101: alu_cnt=4'b0111; //srai
6'b11x010: alu_cnt=4'b1000; //slti
6'b11x011: alu_cnt=4'b1011; //sltiu
```

Instruction Type	Operation	ALU control deciding signal
R	ADD	100000
R	SUB	101000
R	XOR	100100
R	OR	100110
R	AND	100111
R	Shift left logical	100001
R	Shift right logical	100101

R	Shift right arithmetic	101101
R	Set less than	100010
R	Set less than unsigned	100011
I	ADDI	11x000
I	XORI	11x100
I	ORI	11x110
I	ANDI	11x111
I	Shift left logical immediate	110001
I	Shift right logical immediate	110101
I	Shift right arithmetic immediate	111101
I	Set less than immediate	11x010
I	Set less than unsigned immediate	11x011
I	Load byte	00xxxx
I	Load half	00xxxx
I	Load word	00xxxx
I	Load byte unsigned	00xxxx
I	Load half unsigned	00xxxx
S	Store byte	00xxxx
S	Store half	00xxxx
S	Store word	00xxxx
SB	Branch ==	01x000
SB	Branch !=	01x001
SB	Branch <	01x100
SB	Branch >=	01x101
SB	Branch < (U)	01x110

Here x means, it can be 0 or 1

ALU

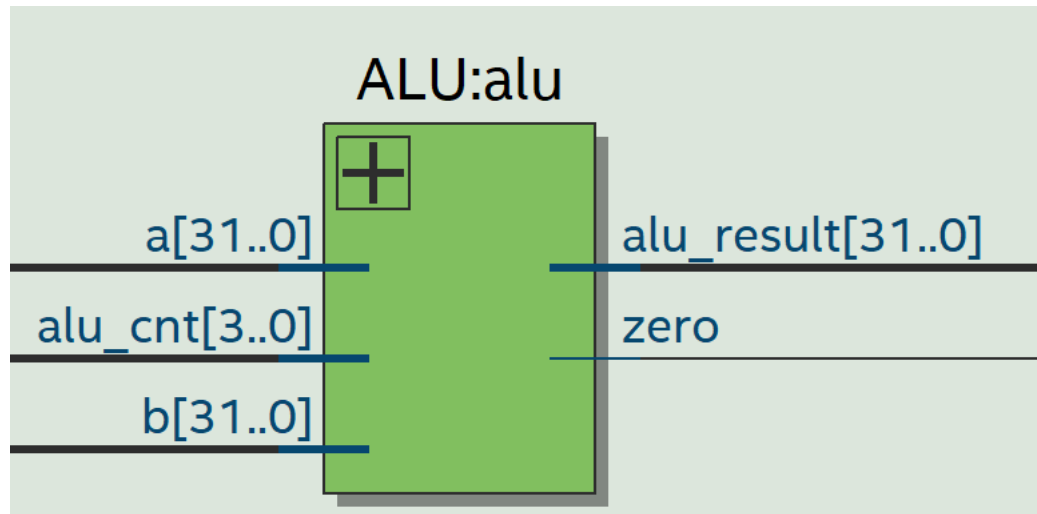

There are three inputs to the ALU. Two of them are operands of the instruction. They are 32 bit long and one of them directly given by the register file while the other input comes through a MUX. Mux decides if it should give the immediate value or the register file value depending on the alu_src control unit output signal. If it is 1 then it selects the immediate value and feed it to the ALU hence otherwise. The following table shows the ALU control signal and the corresponding operation.

Let “a” and “b” be the signed numbers and “A” and “B” be the unsigned numbers


ALU control signal	Operation
0000	$a+b$
0001	$a-b$
0010	$a \wedge b$
0011	$a b$
0100	$a \& b$
0101	$a \ll b$
0110	$a \gg b$
0111	$a \ggg b$
1000	$(a < b) ? 32'd1 : 32'd0$
1001	$(a \neq b) ? 32'd0 : 32'd1$
1010	$(a < b) ? 32'd0 : 32'd1$
1011	$(A < B) ? 32'd0 : 32'd1$

```

4'b0000: alu_result= a+b;//add
      4'b0001: alu_result= a-b;//sub
      4'b0010: alu_result= a^b;//XOR
      4'b0011: alu_result= a|b;//OR
      4'b0100: alu_result= a&b;//AND
      4'b0101: alu_result=a<<b;//shift left Logical
      4'b0110: alu_result=a>>b;//shift right logical
      4'b0111: alu_result=a>>>b;//shift right arithmetic
      4'b1000: begin if (a<b) alu_result=32'd1;else
alu_result=32'd0;end //set less than
      4'b1001: begin if (a!=b) alu_result=32'd0;else
alu_result=32'd1;end
      4'b1010: begin if (a<b) alu_result=32'd0;else
alu_result=32'd1;end
      4'b1011: begin if (A<B) alu_result=32'd1;else
alu_result=32'd0;end//set less than unsigned


```

Program Counter

 

Register, increment by 4 in each clock cycle except both zero and branch control signals are activated. If both zero and branch control signals are activated, PC increment with the desired immediate value (1 bit left shifted imm)

Register File

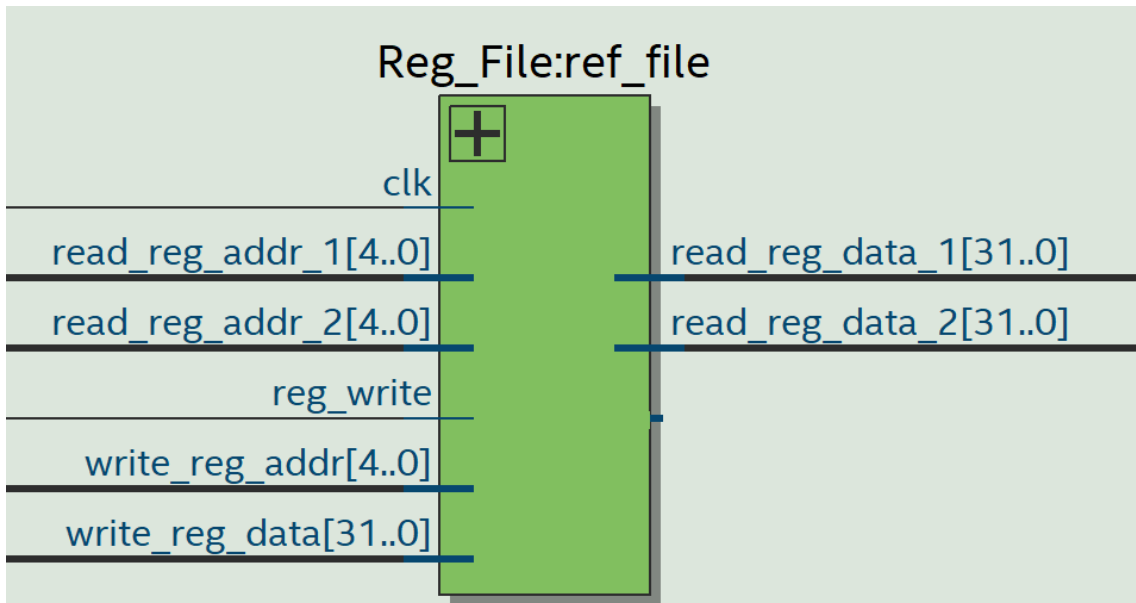

Implemented as array of 32 bits registers which contains 32 registers. X0 is always zero. Other registers can read and write. It has 3 of 5bit address inputs , 32bit data input, 2 of 32bit data outputs and 1bit control signal to activate write operation Read data in the regfile is implemented as combination logic. Register write done at the rising edge of the clock input. when the write signal is activated.


Cache Memory

- 64 Byte Cache
- 16 Byte Victim Cache
- Direct Mapped Cache

One word consists of four bytes



 One cache block consists of four data words



In the cache there are four cache blocks like above.

In the victim cache there is one cache blocks like above.

Other registers:

- Cache tag register – to store the tags of cache blocks
- Victim tag register – to store the tag of victim cache blocks
- Cache valid register – to indicate stored in the cache blocks are valid or not
- Victim valid register – to indicate stored data in the victim cache block is valid or not
- Temporary register – a buffer register that stores data temporarily
- Temporary tag register – a register that stores the tag of the data block in temporary register

Read data:

- Check whether the required data is available in the cache. If it is available, read data from there.
- If the required data is not available in the cache. Check whether the data is available in the victim cache. If data is available there. Load the data into a buffer register. The data available currently in the relevant cache block for expected data moved to victim cache. Then the data in the buffer is moved to the relevant cache block.
- If the data is not available in either cache or victim cache. The expected data is loaded from the data memory to the relevant cache block. And then read the data from there.

Write data:

- Check whether the required data is available in the cache. If it is available, write the data into the cache and then update the relevant memory block.
- If the required data is not available in the cache. Check whether the data is available in the victim cache. If data is available there. Swap the data in the victim cache and the relevant cache block. Write the data into the cache and then update the relevant memory block.
- If the data is not available in either cache or victim cache. The expected data is loaded from the data memory to the relevant cache block. Write the data into the cache and then update the relevant memory block.

Resource Usage

Flow Summary

 <<Filter>>

Flow Status	Successful - Sun Feb 12 15:56:39 2023
Quartus Prime Version	20.1.1 Build 720 11/11/2020 SJ Lite Edition
Revision Name	hydra
Top-level Entity Name	CPU_Demo
Family	Cyclone IV E
Device	EP4CE115F29C7
Timing Models	Final
Total logic elements	7,612 / 114,480 (7 %)
Total registers	5549
Total pins	121 / 529 (23 %)
Total virtual pins	0
Total memory bits	8,192 / 3,981,312 (< 1 %)
Embedded Multiplier 9-bit elements	0 / 532 (0 %)
Total PLLs	0 / 4 (0 %)

Achieved performance level

Slow 1200mV 0C Model Fmax Summary

 <<Filter>>

	Fmax	Restricted Fmax	Clock Name	Note
1	92.42 MHz	92.42 MHz	altera...ed_tck	

Slow 1200mV 85C Model Fmax Summary

 <<Filter>>

	Fmax	Restricted Fmax	Clock Name	Note
1	85.84 MHz	85.84 MHz	altera...ed_tck	


Practically archived Fmax = 50MHz

(We used DE2-115 which has max 50MHz clock source)

Demonstration

Following sample code was used which covers all the supported instruction types. Then all the instructions were converted to machine code and loaded into the instruction memory. Value of x3 is displayed on the 7-segment display. So x3 value is the result.

addi x1,x0,5	# I	
addi x2,x0,12	# I	
add x3, x1, x2	# R	result = h11 (hexadecimal 11)
addi x2, x0, -9	# I	
sub x3, x3, x2	# R	result = h1A
xor x3, x3, x1	# R	result = h1F
addi x4, x0, 10	# I	
or x1, x1, x4	# R	result(stored in x1) = hF
and x3, x3, x1	# R	result = hF
addi x5, x0, 1	# I	
sll x3, x3,x5	# R	result = h1E
srl x4, x4, x	# R	result(stored in x4) = h5
xori x4, x4, 24	# I	result(stored in x4) = h1D
sw x4, 77(x1)	# S	result = h1D is stored in memory address 92
lw x3, 77(x1)	# I(load)	result = h1D
addi x6, x0, 29	# I	
beq x3, x6, 8	# SB	
addi x3, x4, 35	# I	result = h40 if x3!=x6
addi x3, x4, 40	# I	result = h45 if x3==x6
slli x3, x3, 10	# I	result = h11400
srli x3, x3, 3	# I	result = h2280
srai x3, x3, 1	# I	result = h1140
blt x6, x3, 8	# SB	
addi x3, x3, 29	# I	
addi x3, x3, 24	# I	result = h1158 (Final Result)
beq x0,x0,0	# SB	Infinite loop

 

Videos of the running demonstration (intentionally reduced the clock speed by dividing clock source to view the result step by step)